

Bal-Un 50:200

SECOND PART

By iw2fnd Lucio

3) Find the impedance Z_0 of the line to be used

The Guanella Bal-Un requires that the transmission line used be:

$$Z_0 = \sqrt{R_p \cdot R_s} = \sqrt{50 \cdot 200} = 100 \text{ Ohms}$$

Transmission lines with a characteristic impedance of 100Ω are typically bifilar lines. They can be constructed, but commercially available conductors for 12V DC (**red**/black) or audio (**blue**/black) have a characteristic impedance of around 100Ω .

4) Select the wire gauge

From an electrical perspective, the Guanella Bal-Un is an up-autotransformer. Therefore, the current passing through the common winding (i_c) is the difference between the primary current (i_p) and the current flowing through the series windings (i_s , which is equal to that of the secondary). In this case, the current passing through the two transmission lines is half of the primary current.

$$i_s = i_c = \frac{1}{2} \sqrt{\frac{P}{Z_p}} = \frac{1}{2} \sqrt{\frac{500}{50}} = 1,58 \text{ A}$$

In the market, there are audio cables of various cross-sections.

Since the current density in the cables is chosen around 2 A/mm². To support a current of 1.58 A, a cable of 1.5 mm² is sufficient. With such a cable, you can wind 8+8 turns on an FT240-61 ferrite.


5) Check the ferrite

Ferrite of grade #61 allows a maximum magnetic flux density of 250 mT. The formula for calculating the flux in a toroid is that of transformers. If the frequency f is in [MHz], the area A_e is in [cm²], the result will be in [mT]:

$$B_{Max} > \frac{10 \cdot V_{eff}}{\sqrt{2} \pi f \cdot n_p \cdot A_e} = \frac{10 \cdot \sqrt{P \cdot Z_p}}{\sqrt{2} \pi f \cdot n_p \cdot A_e} = \frac{10 \cdot \sqrt{500 \cdot 50}}{4,44 \cdot 7 \cdot 16 \cdot 1,58} = 2,01 \text{ mT}$$


From this, it can be seen that the maximum flux density allowed in the ferrite is much higher than that generated by the transmitted power P of 500W.

6) Construct the Bal-Un

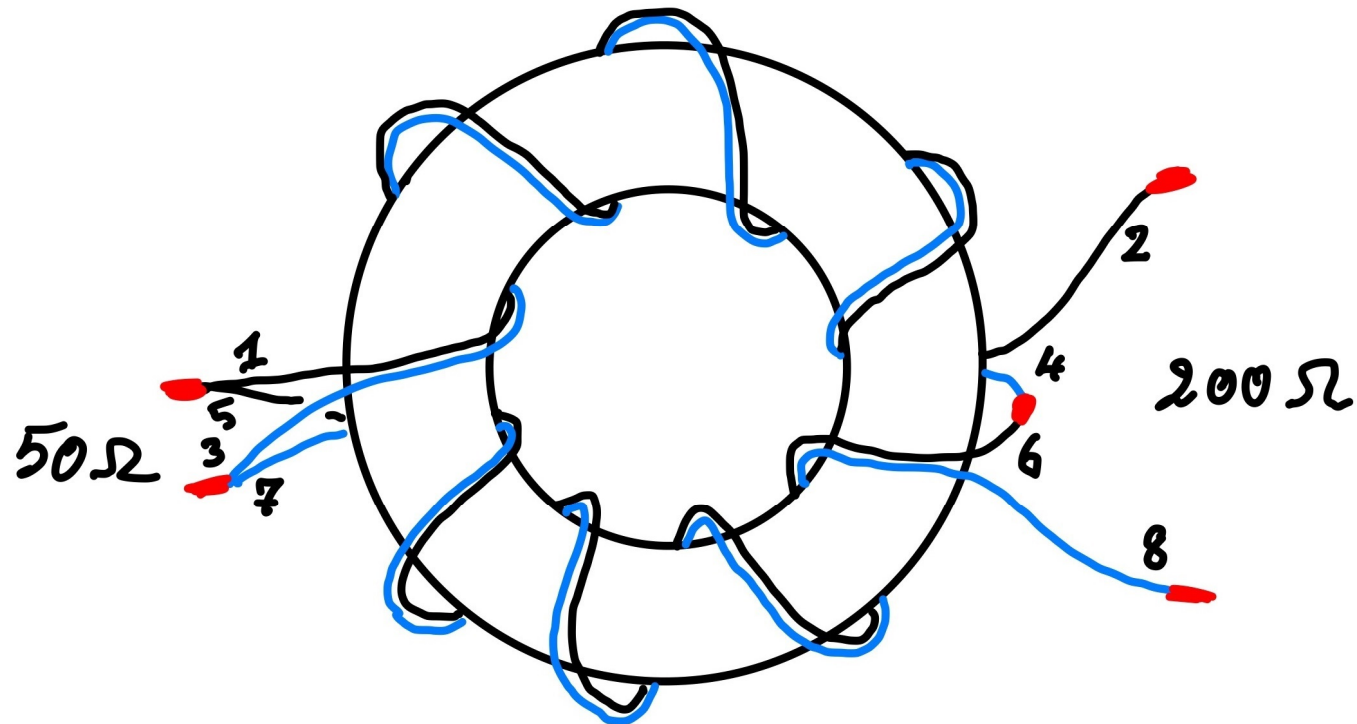


8+8 turns of bifilar transmission line $Z_0 = 100\ \Omega$,
on FT240-61 ferrite.

7) Test the Bal-Un with a VNA

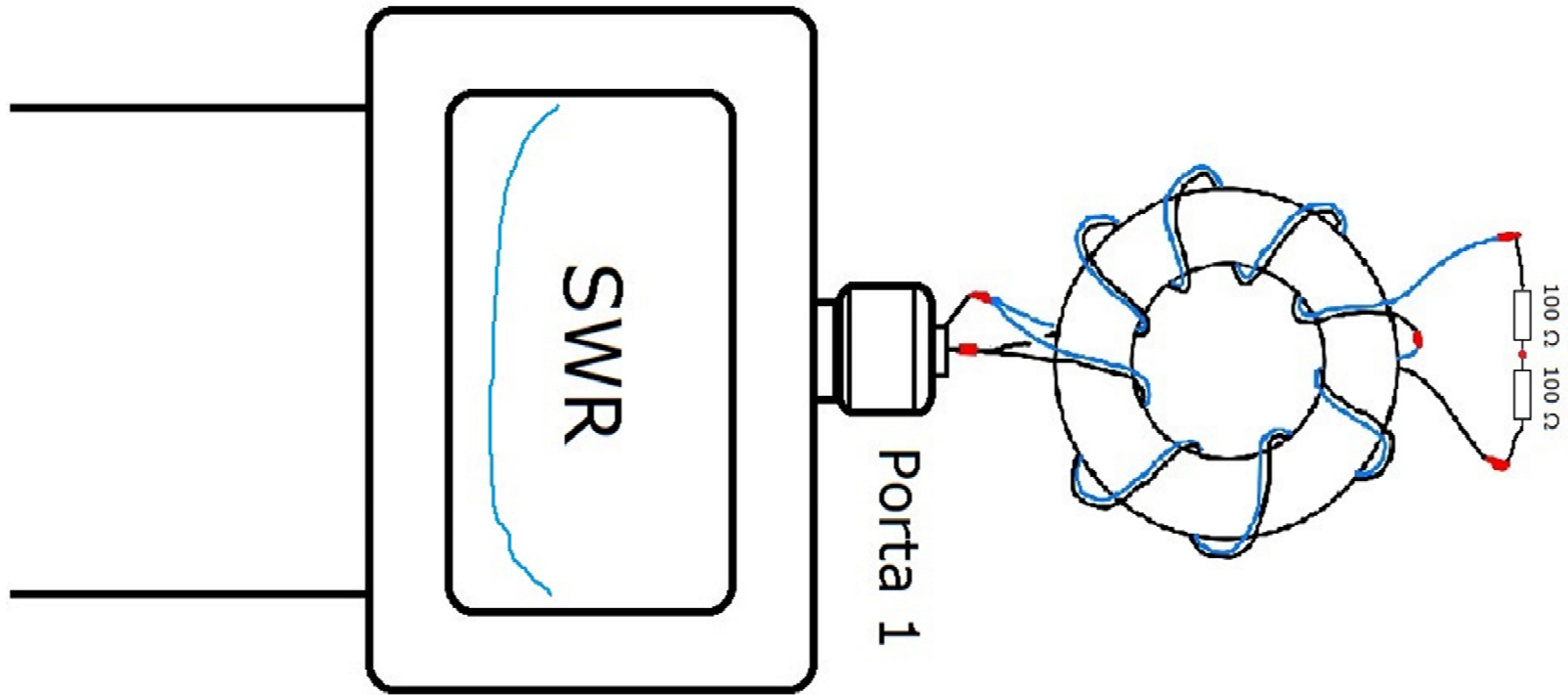


7) Test the Bal-Un with a VNA

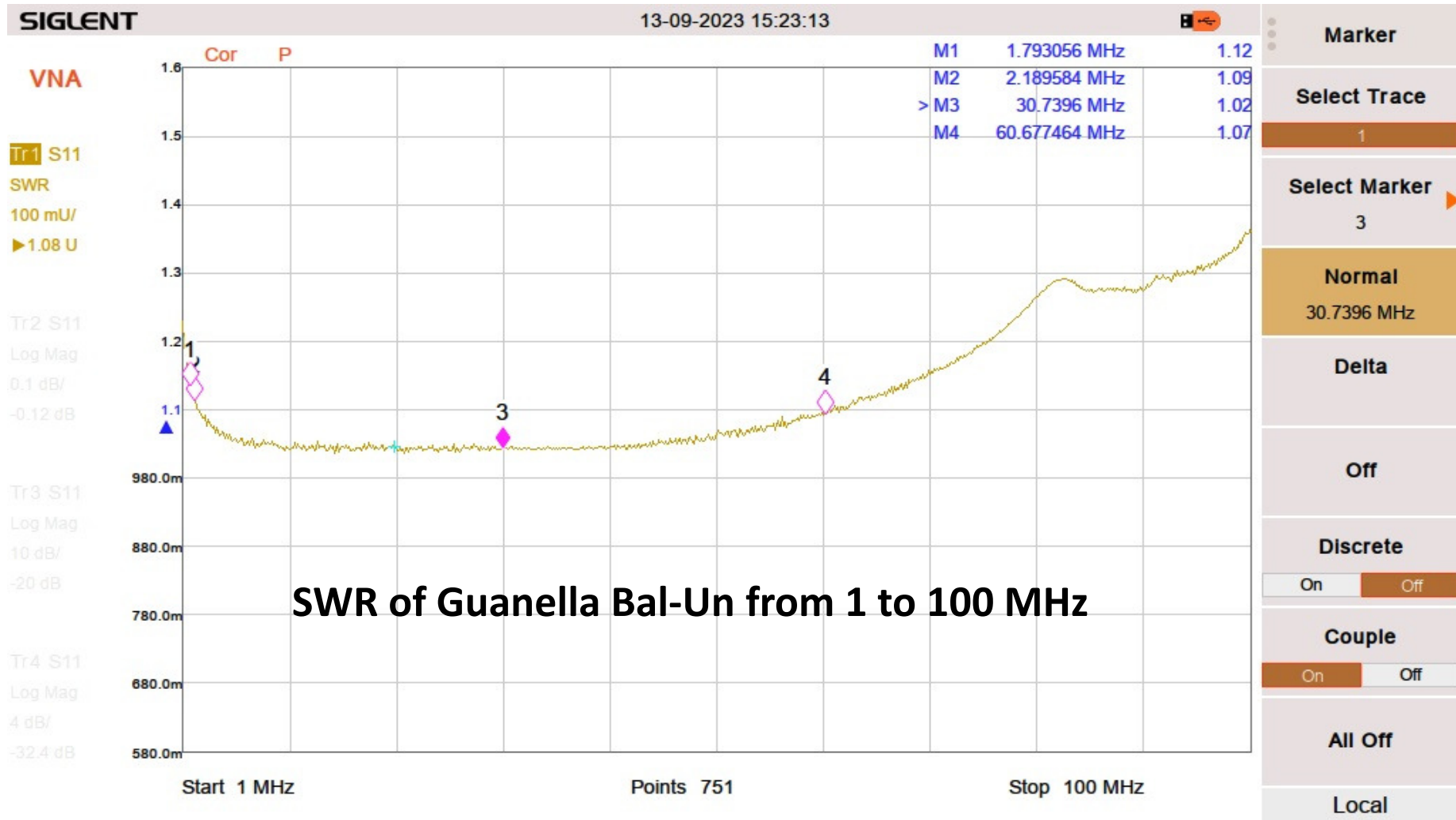

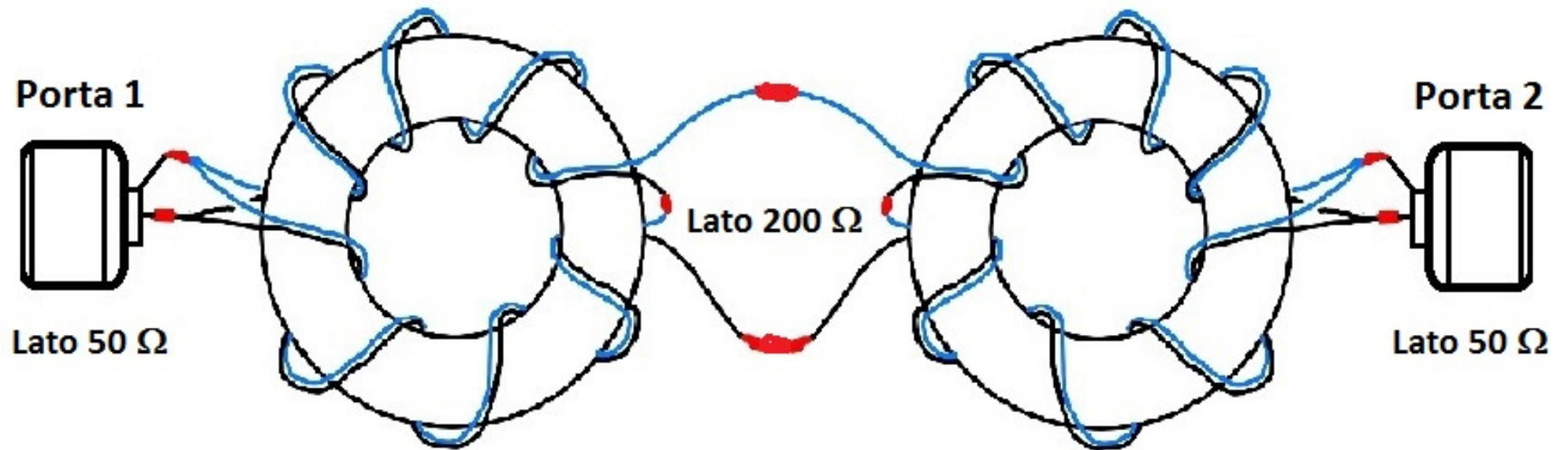7) Test the Bal-Un with a VNA

Set-up per la misura della perdita d'inserzione S21



7) Test the Bal-Un with a VNA

